

APPLICATION OF DIFFERENTIAL EQUATIONS

Q.1 A chain coiled up near the edge of a smooth table starts to fall over the edge. The velocity v when a length x has fallen is given by $xv \frac{dv}{dx} + v^2 = gx$. Solve the Differential equation to express v in terms of x .

Solution: The given differential equation is $xv \frac{dv}{dx} + v^2 = gx$ (1)

$$\text{put } v^2 = y \quad \therefore 2v \frac{dv}{dx} = \frac{dy}{dx}$$

$$\therefore \text{From (1)} \quad x \left(\frac{1}{2} \frac{dy}{dx} \right) + y = gx$$

$$\therefore \frac{dy}{dx} + \left(\frac{2}{x} \right) y = 2g$$

It is linear differential equation with $P = \frac{2}{x}$ and $Q = 2g$

$$\therefore \text{Its solution is } ye^{\int P dx} = \int Q \cdot e^{\int P dx} dx + c$$

$$ye^{\int \frac{2}{x} dx} = \int 2g \cdot e^{\int \frac{2}{x} dx} dx + c$$

$$yx^2 = \int 2g \cdot x^2 dx + c$$

$$yx^2 = \frac{2}{3} gx^3 + c$$

$$v^2 x^2 = \frac{2g}{3} x^3 + c$$

Q.2. In a circuit containing inductance L , resistance R , and voltage E , the current i is given by

$$L \frac{di}{dt} + Ri = E. \text{ Find the current } i \text{ at time } t \text{ if at } t = 0, i = 0 \text{ and } L, R, E \text{ are constants.}$$

Solution: The given equation $\frac{di}{dt} + \frac{Ri}{L} = \frac{E}{L}$ is linear of the type $\frac{dy}{dx} + Py = Q$

$$\therefore \text{Its solution is } i \cdot e^{\int (R/L) dt} = \int \frac{E}{L} \cdot e^{\int (R/L) dt} dt + c$$

$$\therefore i \cdot e^{Rt/L} = \frac{E}{L} \int e^{Rt/L} dt + c = \frac{E}{L} \cdot e^{Rt/L} \cdot \frac{L}{R} + c = \frac{E}{R} e^{Rt/L} + c$$

$$\text{When } t = 0, i = 0 \quad \therefore c = -\frac{E}{R}$$

$$\therefore i \cdot e^{Rt/L} = \frac{E}{R} e^{Rt/L} - \frac{E}{R} = \frac{E}{R} (e^{Rt/L} - 1)$$

$$\therefore i = \frac{E}{R} (1 - e^{-Rt/L})$$

Q.3. In a circuit containing inductance L resistance R and voltage E , the current i is given by

$$E = Ri + L \frac{di}{dt}. \text{ If } L = 640 \text{ h}, R = 250 \Omega \text{ and } E = 500 \text{ volts and } i = 0 \text{ when } t = 0, \text{ find the time that elapses before the current reaches 90\% of its maximum value.}$$

Solution: As in above example the current is given by $i = \frac{E}{R} (1 - e^{-Rt/L})$

Maximum value of i is I , can be obtained when $t \rightarrow \infty$

$$\therefore I = \frac{E}{R} (1 - 0) = \frac{E}{R}$$

$$\text{When } i = 90\% \text{ if } I = \frac{9}{10} I = \frac{9E}{10R}$$

$$\text{We get } \frac{9E}{10R} = \frac{E}{R} (1 - e^{-Rt/L})$$

$$\frac{9}{10} = 1 - e^{-Rt/L}$$

$$e^{-Rt/L} = 1 - \frac{9}{10} = \frac{1}{10}$$

$$e^{Rt/L} = 10$$

$$Rt/L = \log 10$$

$$t = \frac{L}{R} \log 10 \text{ sec}$$

$$\therefore t = \frac{640}{250} \log 10 = 5.89 \text{ sec}$$

Q.4. The charge q on the plate of a condenser of capacity C charged through a resistance R by the steady voltage V satisfies the differential equation $R \frac{dq}{dt} + \frac{q}{C} = V$. If $q = 0$ at $t = 0$, show that $q = CV(1 - e^{-t/RC})$. Find also the current flowing into the plate.

Solution: We are given that $\frac{dq}{dt} + \frac{1}{RC} \cdot q = \frac{V}{R}$

This is a linear differential equation of the type $\frac{dy}{dx} + Py = Q$

Its solution is $q \cdot e^{\int(1/RC)dt} = \int e^{\int(1/RC)dt} \cdot \frac{V}{R} dt + k$

$$\therefore q \cdot e^{t/RC} = \int e^{t/RC} \cdot \frac{V}{R} dt + k = \frac{V}{R} \cdot \frac{e^{t/RC}}{(1/RC)} + k$$

By data when $t = 0, q = 0 \quad \therefore k = -CV$

$$\therefore q \cdot e^{t/RC} = CV \cdot e^{t/RC} - CV = e^{t/RC} (CV - CV e^{-t/RC})$$

$$\therefore q = CV(1 - e^{-t/RC})$$

$$\text{Further } i = \frac{dq}{dt} = CV \cdot e^{-t/RC} \cdot \frac{1}{RC} = \frac{V}{R} \cdot e^{-t/RC}$$

Q.5. An equation in the theory of stability of an aeroplane is $\frac{dv}{dt} = g \cos \alpha - kv$, v being velocity and g, k being constants. It is observed that at time $t = 0$, the velocity $v = 0$. Solve the equation completely.